



שפת תכנון חומרה –

Verilog

מטלה מספר 4

מגיש :

חיים עוזר - 316063569

מכונת מצבים MooreArbiter

❖ Code:

```
module MooreArbiter (
    input wire CLK,RESET,req0,req1,req2,req3,
    output reg grant0,grant1,grant2,grant3);

// Define states
reg [2:0] currentState, nextState;

// State constants
parameter IDLE_STATE = 3'b000;
parameter GRANT_STATE_0 = 3'b001;
parameter GRANT_STATE_1 = 3'b010;
parameter GRANT_STATE_2 = 3'b011;
parameter GRANT_STATE_3 = 3'b100;

// logic for next state and outputs
always @(*) begin
    grant0 = (currentState == GRANT_STATE_0);
    grant1 = (currentState == GRANT_STATE_1);
    grant2 = (currentState == GRANT_STATE_2);
    grant3 = (currentState == GRANT_STATE_3);

    // Default next state
    nextState = currentState;

    // State transitions
    case (currentState)
        IDLE_STATE:
            if (req0) begin
                nextState = GRANT_STATE_0;
            end
            else if (req1) begin
                nextState = GRANT_STATE_1;
            end
            else if (req2) begin
                nextState = GRANT_STATE_2;
            end
            else if (req3) begin
                nextState = GRANT_STATE_3;
            end
            end

        GRANT_STATE_0: begin
            if (!req0) begin
                nextState = IDLE_STATE;
            end
            end

        GRANT_STATE_1: begin
            if (!req1) begin
                nextState = IDLE_STATE;
            end
            end

        GRANT_STATE_2:begin
            if (!req2) begin
                nextState = IDLE_STATE;
            end
            end

        GRANT_STATE_3:begin
            if (!req3) begin
```

```

        nextState = IDLE_STATE;
    end
end


    default: nextState = IDLE_STATE;
endcase
end

// Sequential logic for state register and synchronous reset
always @(posedge CLK) begin
    if (RESET) begin
        currentState <= IDLE_STATE;
    end
    else begin
        currentState <= nextState;
    end
end


endmodule

```


❖ RTL:

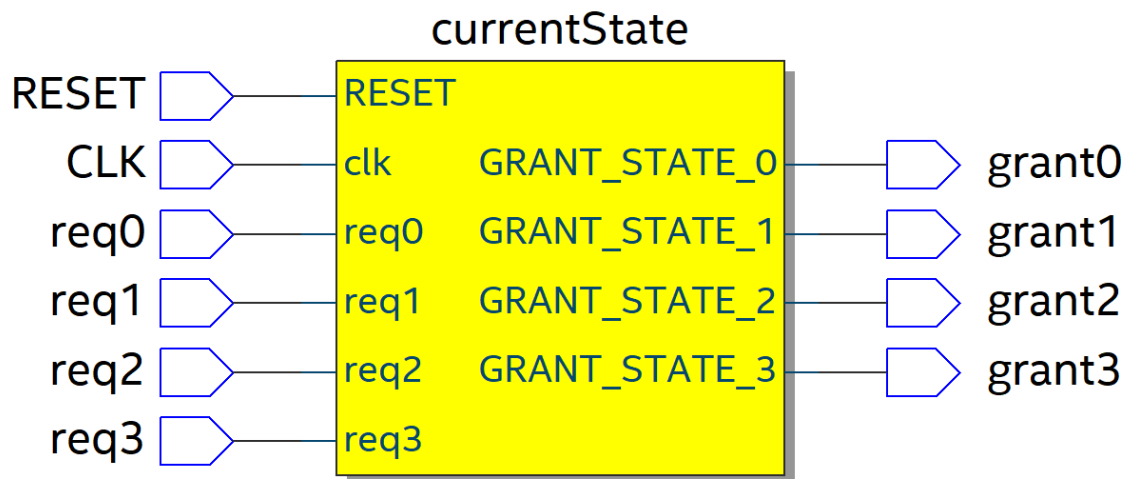

❖ State Machine

 

❖ Compilation:

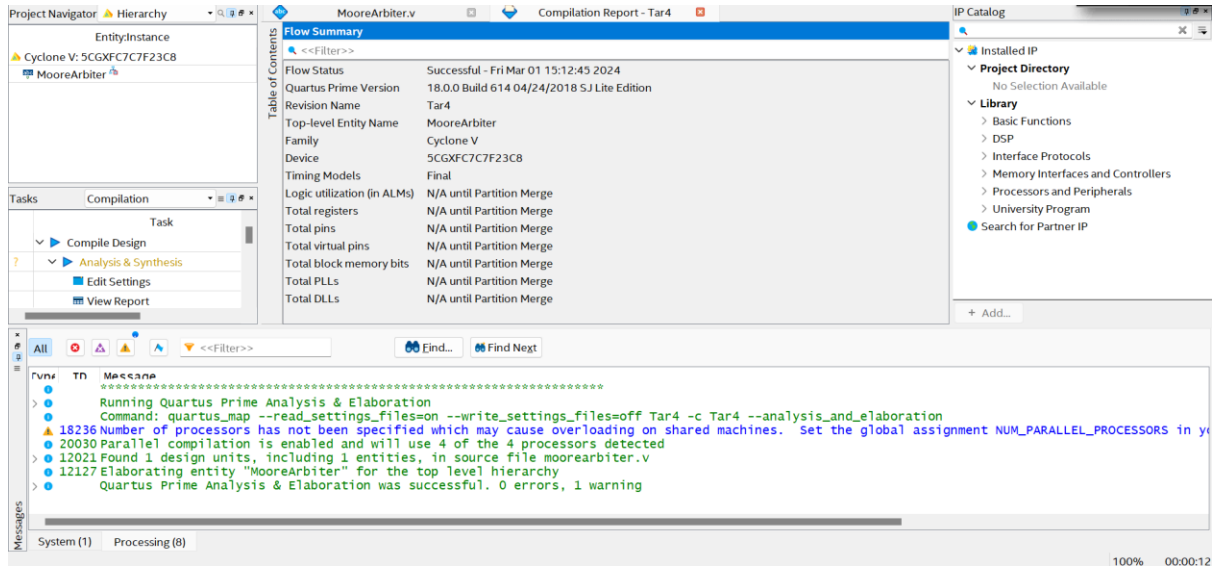

Test Bench:

❖ Code:

```
`timescale 1ns / 1ps

module MooreArbiter_tb;

    reg clock;
    reg reset;
    reg [3:0] request;
    wire [3:0] grant;
    Arbiter uut (
        .clock(clock),
        .reset(reset),
        .request(request),
        .grant(grant)
    );
    reg [3:0] request_sequence[7:0];
    integer i;
    initial begin
        clock = 0;
        forever #10 clock = ~clock; // 50 MHz clock
    end
    initial begin
        reset = 1;
        request = 4'b0000;
        #20;
        reset = 0;

        request_sequence[0] = 4'b0001;
        request_sequence[1] = 4'b0010;
        request_sequence[2] = 4'b0100;
        request_sequence[3] = 4'b1000;
        request_sequence[4] = 4'b0011;
        request_sequence[5] = 4'b0110;
        request_sequence[6] = 4'b1100;
        request_sequence[7] = 4'b0000;
        for (i = 0; i < 8; i = i + 1) begin
            request = request_sequence[i];
        end
    end
endmodule
```

```

#20;
end

$finish;
end

endmodule

```

❖ Wave – Model sim:

